



life.augmented

# An approach to practical digital power conversion

Ranajay MALLIK

STMicroelectronics

- Why digital
- Moving from analog to digital
- LLC converter realization
  - Power plant, modulator, feedback management, protections
- Typical gain curve for wide output voltage range LLC converters
- 2.5 kW LEV battery charger details
- 6 kW DC DC converter

# Why digital power (1)

- Digital power applications use digitally controlled solutions:
  - To increase power density
  - To accelerate control loops
  - To allow complex topology management, otherwise impossible with analog control
  - To significantly improve design flexibility
- **Prototyping changes can be faster : instead of changing the hardware design, we change the code to try out a better or evolved control scheme**

# Why digital power (2)

- Facilitates compliance with the most stringent energy efficiency requirements
  - By using clever algorithms, light load and switching patterns may be handled in a way to reduce losses
- Greater power density with higher switching frequency and faster control loops
  - With advanced wide band gap devices higher switching frequencies mean faster decisions to be made in nanoseconds
- System level reliability, and safety with failure prediction in power distribution
  - Model predictive control, AI and ML lends itself well to manage futuristic power conversion systems

# Where do we find them?

- Mostly applied to switched-mode power supplies (SMPS)
- Digital power focuses mainly on solutions for:
  - Server and datacenters PSUs
  - Telecom power
  - EV charging stations
  - UPS, energy generation & storage systems
  - Recently adopted in sophisticated chargers and adapters for smartphones and laptops in high-end TV and lighting applications.
- Found earlier in high-performance, high-end systems but with new efficiency norms found in almost all power supply types

# Moving from analog to digital design

- Pure analog
  - Use dedicated single or dual function controllers
- Hybrid: mixed analog + digital control
  - Dedicated analog controllers with one inner control loop (analog)
  - One digital controller (MCU) for outer loop
- Full-digital
  - Completely digital
  - Sensing, computing and decision making (acting)

# LLC converter realization

## Major philosophy

**LLC converter** is well known for its high efficiency, low EMI content and simple modulation scheme: PFM instead of PWM

Design however has these dimensions which must all be addressed together

- **Power plant design**
  - Topology, magnetics and the tank, switches and rectifiers
- **Modulator design**
  - VCO, phase shifter, dead-time generation and interlocking functions
- **Feedback management**
  - Voltage feedback? current feedback? error amplifier and its order stability: how fast, is it fast enough?
- **Protections**
  - Startup management, operating zones and anti capacitive region management, functional protections inherent to topology

This is 100% analog block!!

Rest can be partially or fully digital

# Power plant - full bridge LLC converter


LLC Resonant Converter

MOSFET key FoM:

- i) Low  $R_{dsON}$
- ii) Controlled  $C_{oss}$

The Tank determines eventual performance

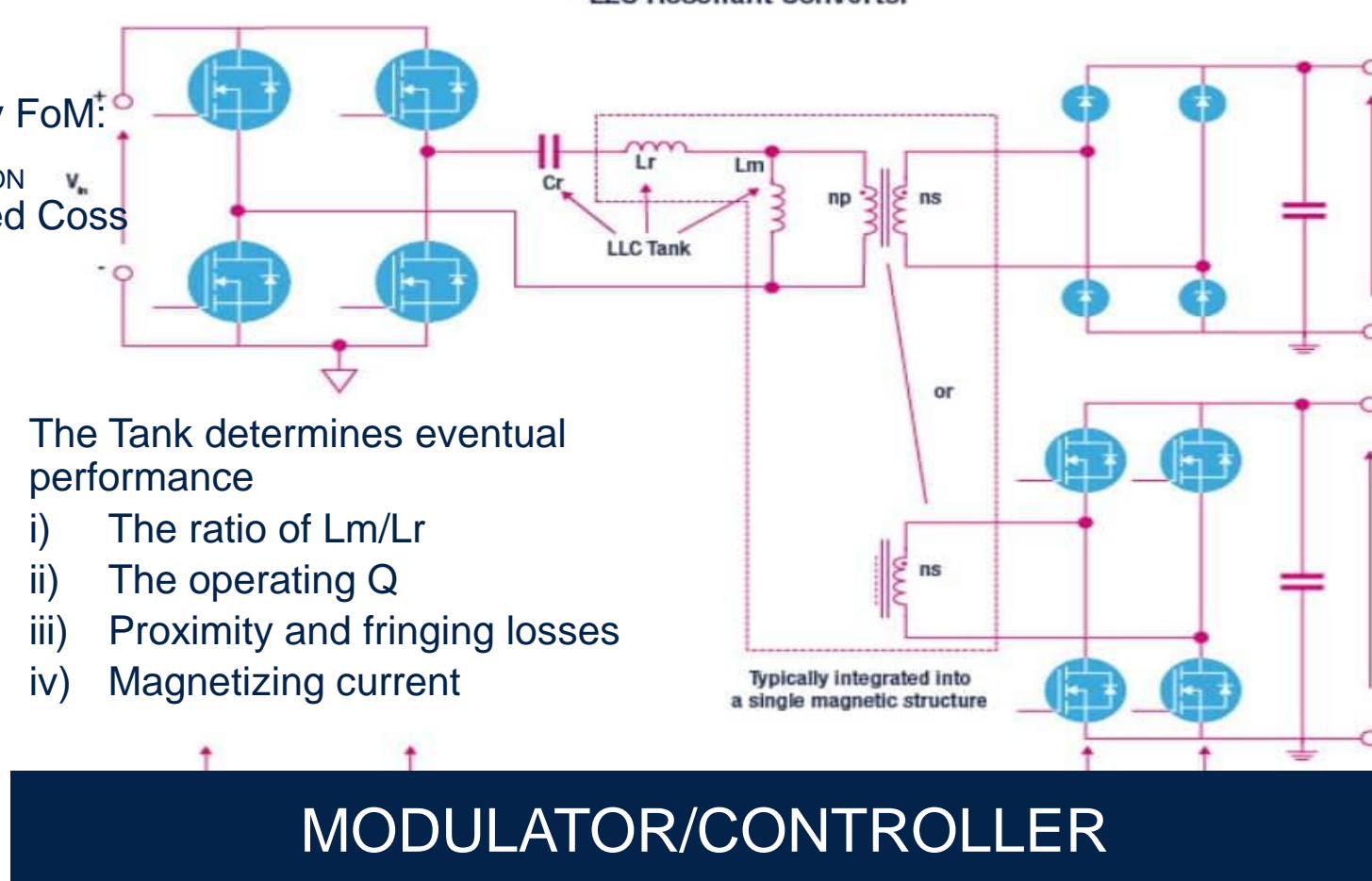- i) The ratio of  $L_m/L_r$
- ii) The operating  $Q$
- iii) Proximity and fringing losses
- iv) Magnetizing current




- i) Low voltage moderate current
- ii) High voltage moderate to high current
- iii) Key FoM: low  $V_f$ , Zero recovery
- iv) Center tap less lossy


- i) Low voltage high current
- ii) High voltage rarely used
- iii) Key FoM: Low  $R_{dsON}$ ,  $Q_g$



# Analog modulator - L6699 controller


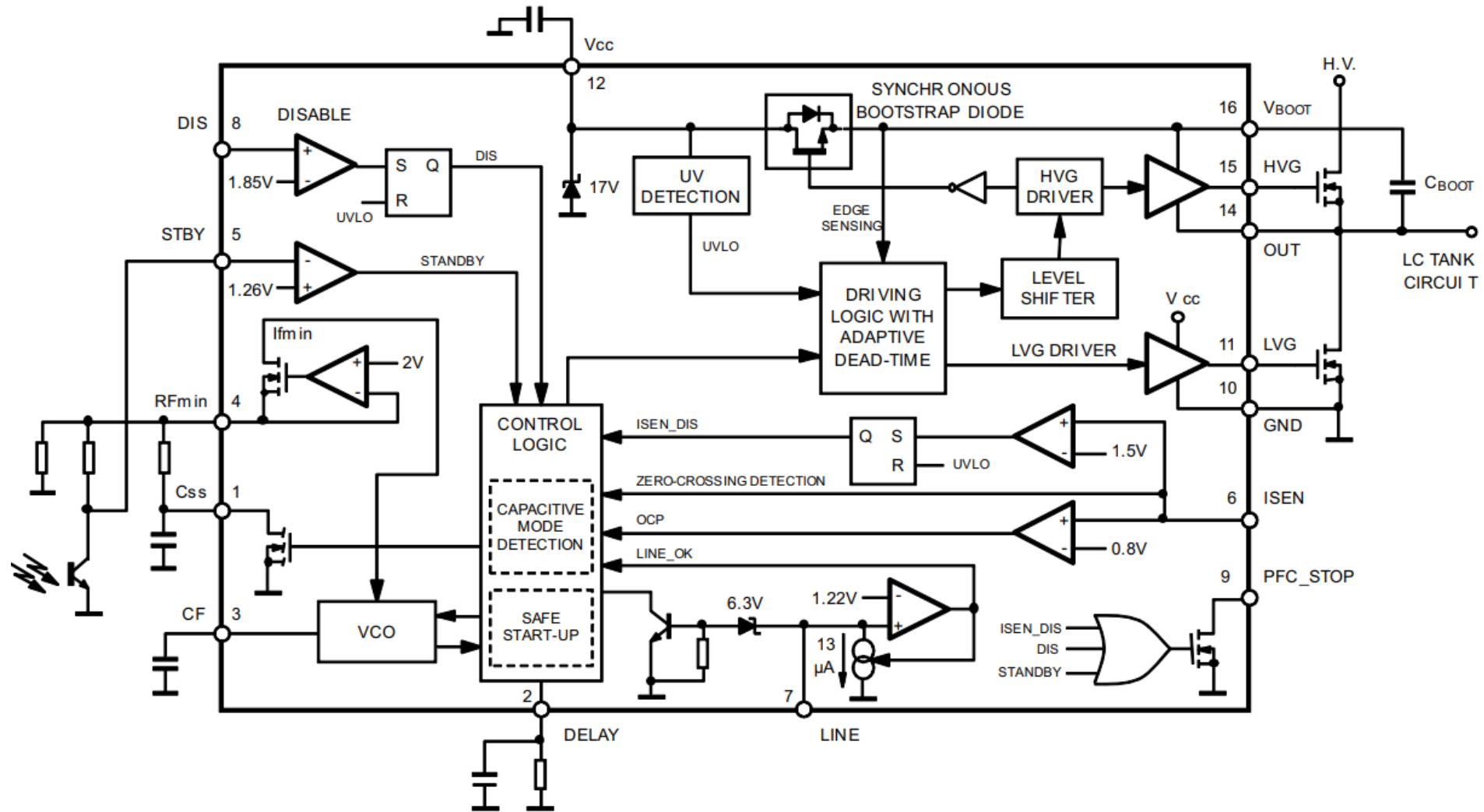

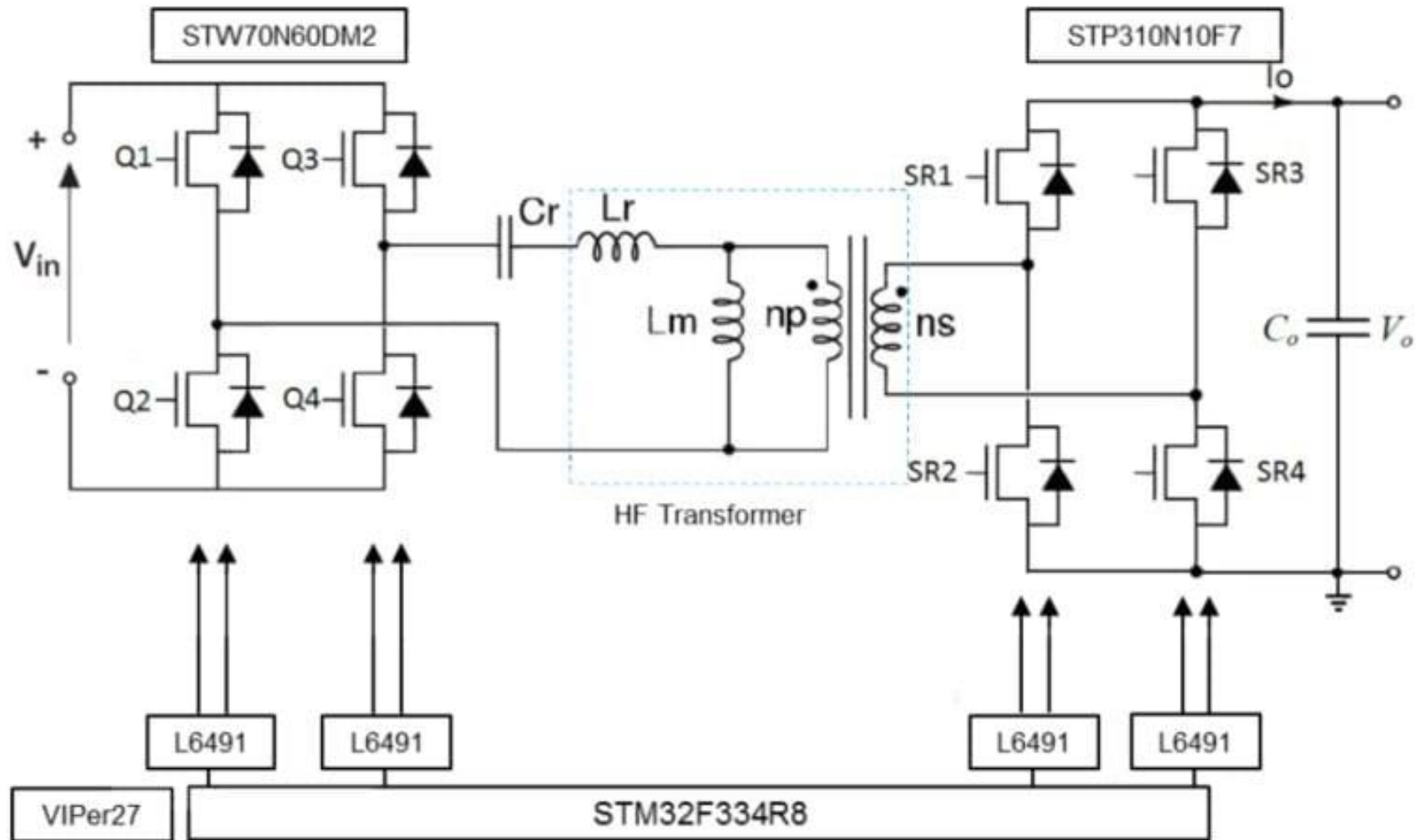
# Digital modulator - implementation scheme



- Start-up sequence and preventing anti capacitive region operation
- Runtime over current/overload/short circuit
- Feedback loop open
- System level protections: over temperature/over voltage/load disconnections etc.
- Addressable in both discrete analog and interrupt/event driven digital formats
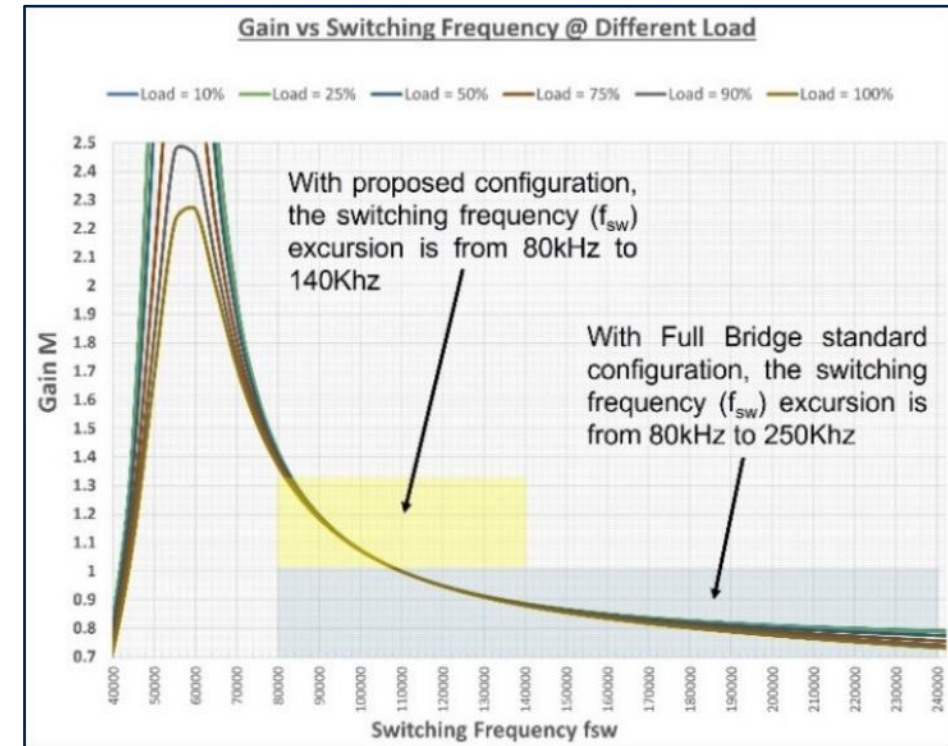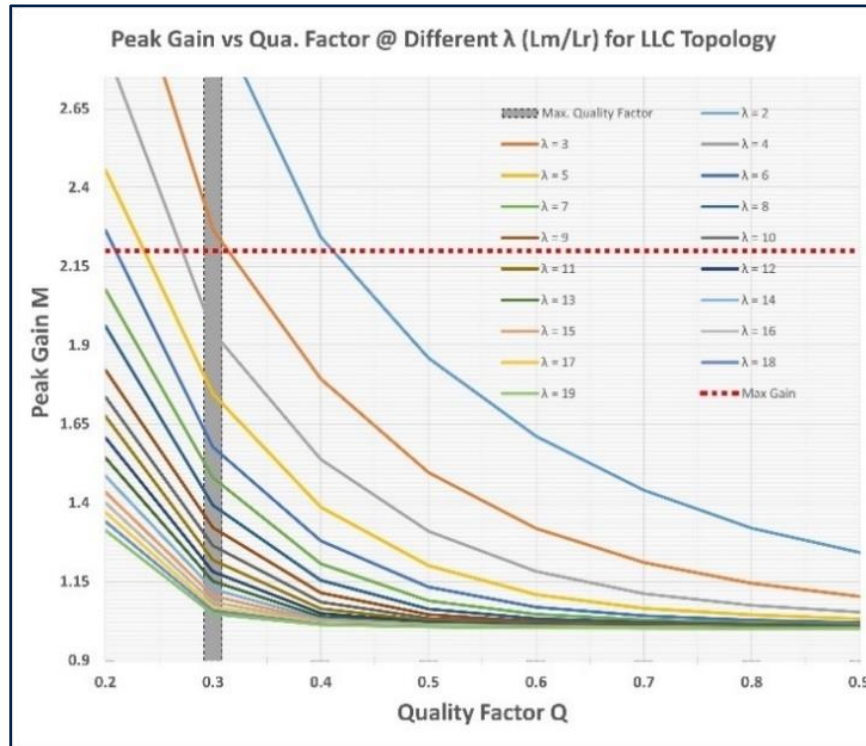
# Tank gain curve and operating point for wide output voltage range




Very important to choose the correct  $Q$ ,  $M$ ,  $F_{min}$ - $F_{max}$  and  $N_p/N_s$ . Important also to consider production tolerances of magnetics in mass manufacturing. Certain digital techniques will circumvent that automatically
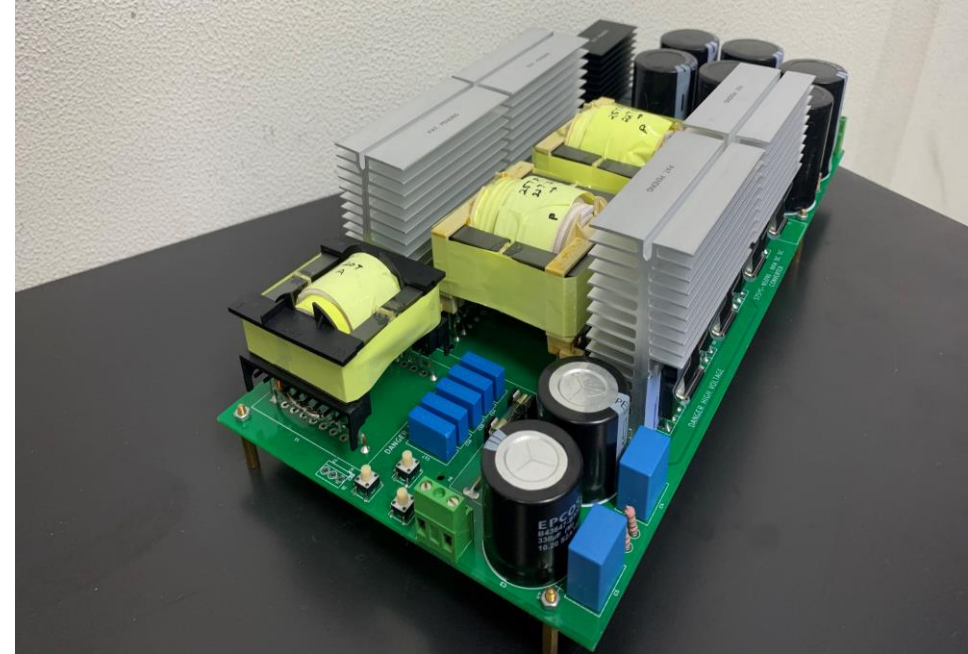
# Real MCU based systems - kW level power converters



2500W light electric vehicle (LEV) charger



6000W wide output range LLC converter

Both MCU based, high performance converters, using LLC topology over a wide output range




# 2.5 kW light electric vehicle (LEV) charger

## Key features

- Multi battery chemistry charger design
- CCM PFC + FB LLC 2.5kW converter
- 110V/230V in, 40-60DC wide output, 40A  $I_o$  max
- Mixed analog and MCU control
- Peak Efficiency 93.5% end to end
- PF>0.95 and THD <5% nominal power
- CAN/RS485 interface for remote configuration
- Comprehensive protection
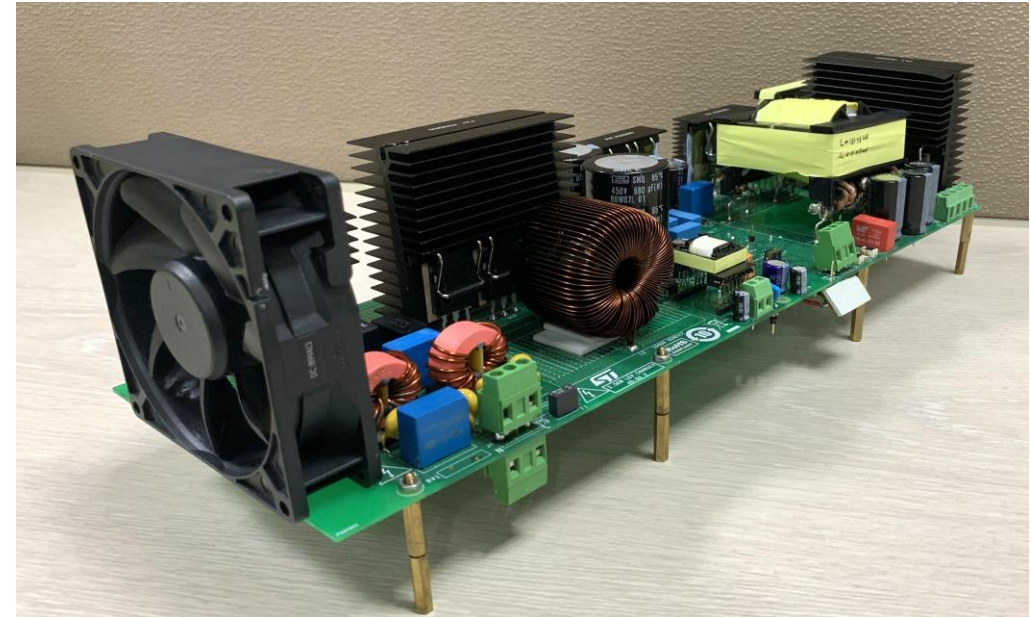
## Applications


- LEV charging
- Li Ion and general battery charger
- SMPS and robotic mobility



## 2.5 kW LEV battery charger



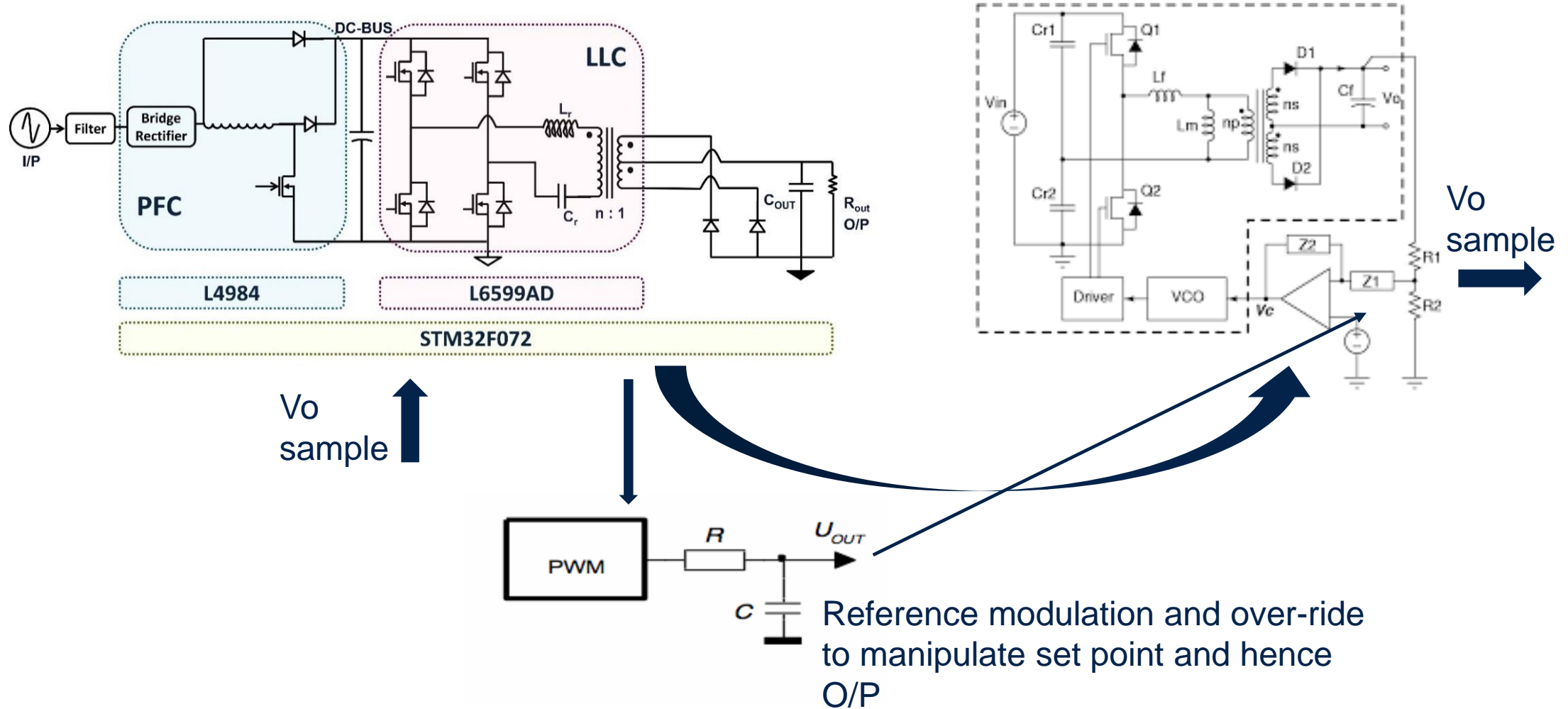
# Hybrid (analog + digital) control scheme






# 2.5 kW LEV battery charger performance details


Pout vs Eff @60V

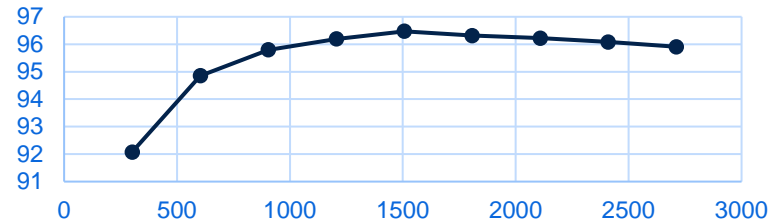


Output Regulation Vout vs Iout  
@60V

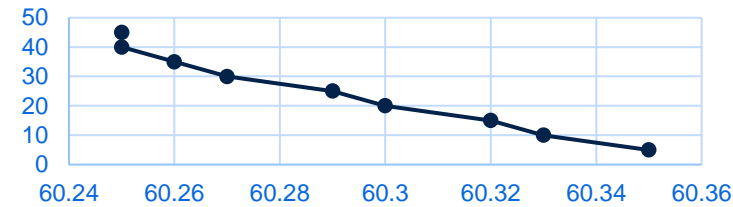


Pout vs Eff @40V

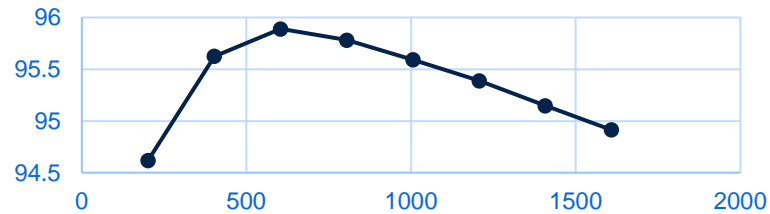


Output Regulation Vout vs Iout  
@52V

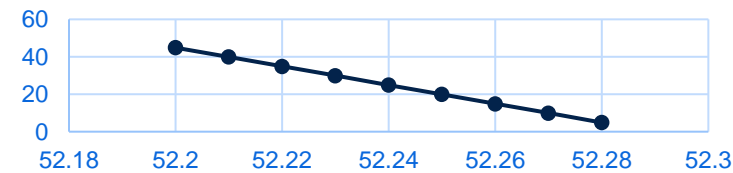

Pout vs Eff @52V

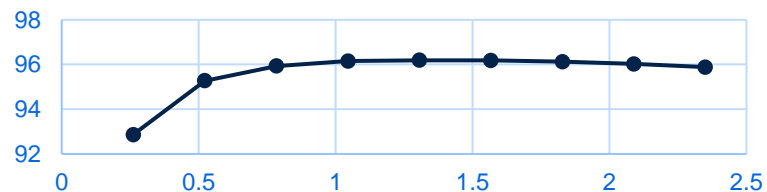

Output Regulation Vout vs Iout  
@40V

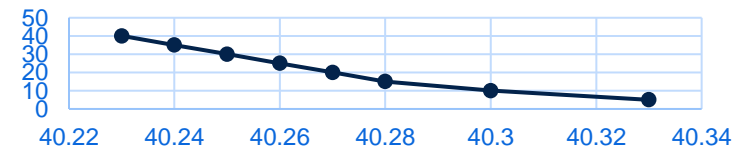

# Thermal performance @ 2.5kW load




TOLL PCB on heatsink




PCB trace heat: PCB is 130C class
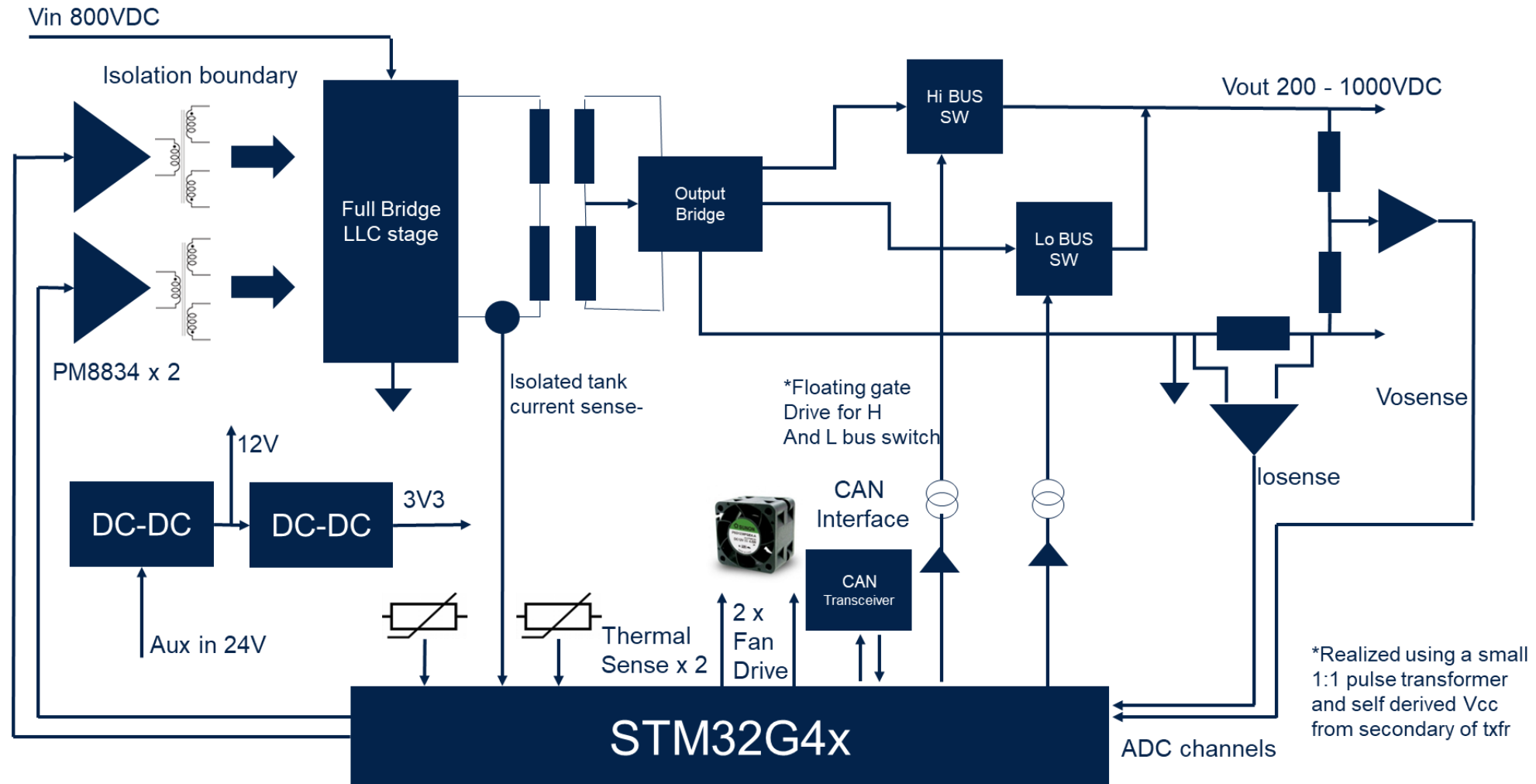
# Block diagram 6 kW DC-DC digitally controlled LLC converter



# Implementation

## Full bridge LLC converter power plant

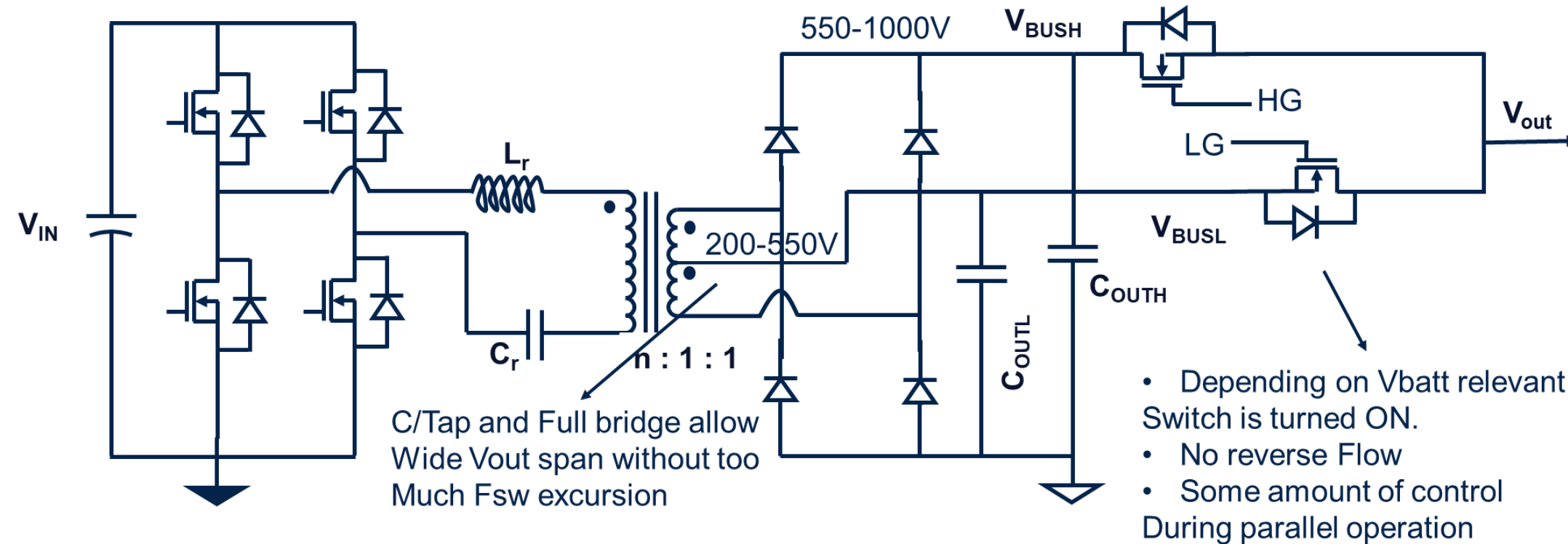

Full Bridge LLC power plant with output doubler configuration

# 6 kW DC-DC converter with wide range output voltage

## Key Features :


- Configuration: full Bridge LLC + full bridge rectification
- 6 kW power output with maximum efficiency > 97.9%
- Input Voltage: 700-800 DC
- Output voltage configuration: 200-1000V
  - Output high side MOSFET ON: 550 – 1000V
  - Output low side MOSFET ON: 200 – 550V
- Unique control technique to address low voltage requirements
- Comprehensive safety and protection mechanism

## Applications:

- Battery charger
- EV applications



# Resonant Tank - operating region

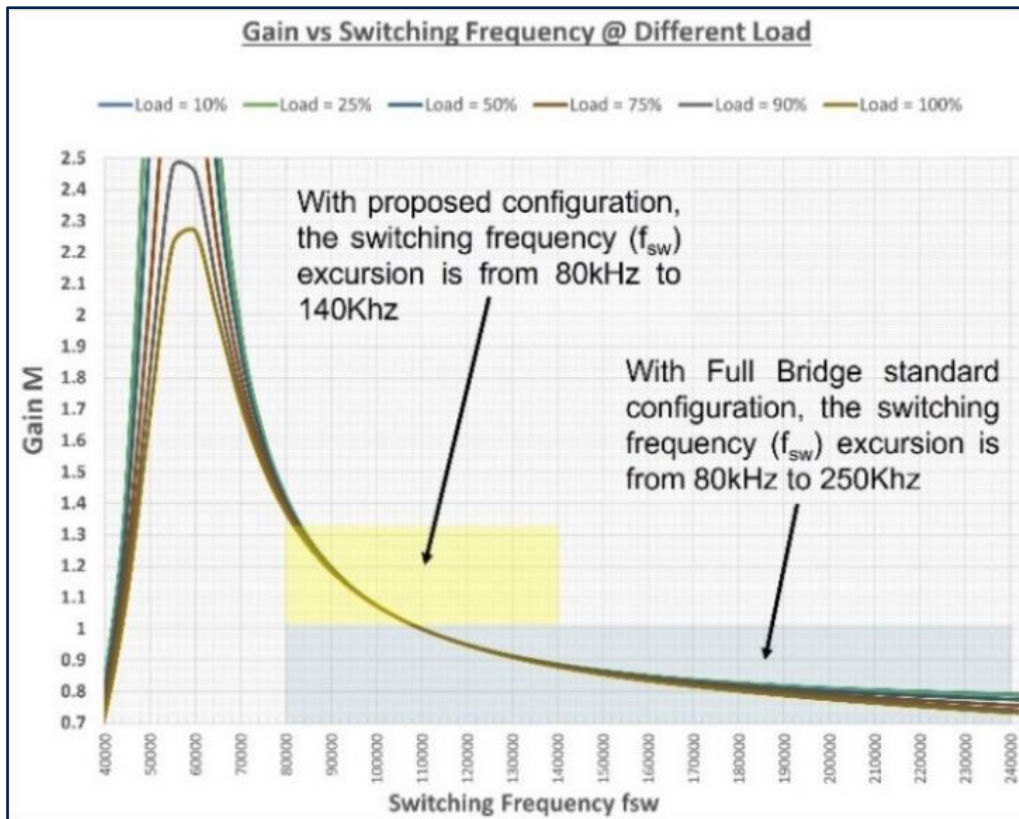


- $F_{res}$ : 110 kHz
- $F_{min}$ : 80 kHz
- $F_{max}$ : 180 kHz(140 kHz)
- $N = 1.08:1:1$
- $Q = 0.32$  nominal
- Gain min = 1.33 Gain max = 2.4
- $V_{in}$  800V
- $P_o = 6000W$
- $V_o = 500-1000VDC$  (effective 200-1000V with margin) tolerance
- $L_m/L_r = 3 \rightarrow$  Low ratio lesser  $F$  span

Very Important choose the correct  $Q$ ,  $M$ ,  $F_{min}$ - $F_{max}$  and  $N_p/N_s$ . important also to consider production tolerances of magnetics in mass manufacturing. Certain digital techniques will circumvent that automatically

# 6kW DC-DC converter simulation performance (1/4)

100% power

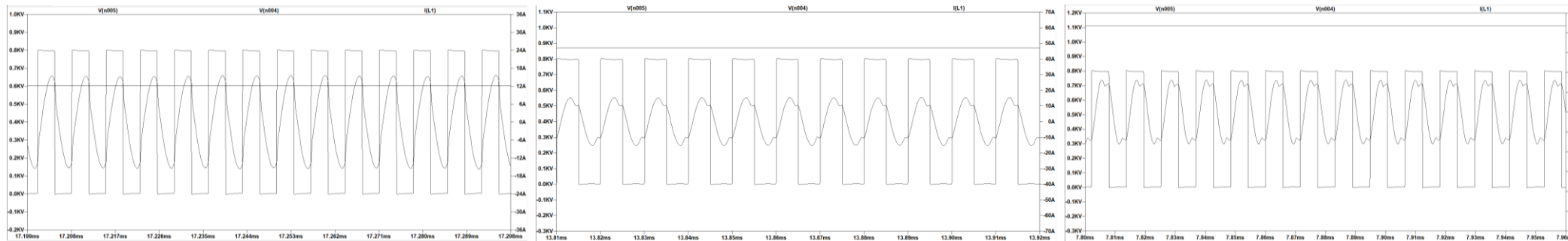


600V 10A 143kHz  
Inductive zone

870V 7A 100kHz  
Slightly left of resonance  $F_r$

1100V 5.7A 86kHz  
Left of resonance  $F_r$

10% power

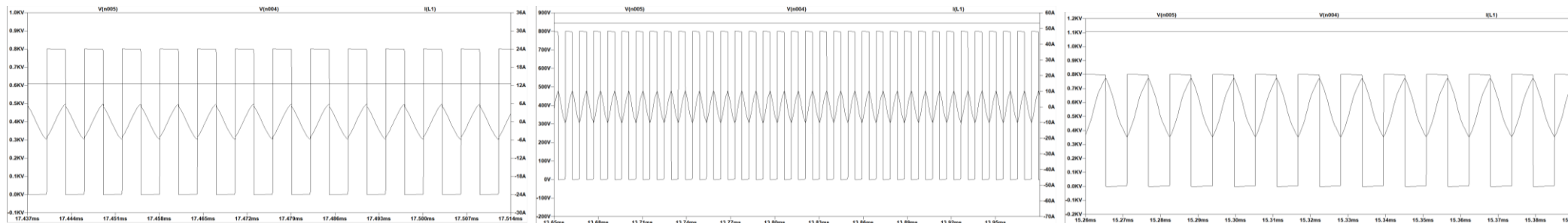

600V 1A 166kHz


870V 0.7A 104kHz

1100V 0.57A 88kHz


\*Lower voltage range behaves identically as it is **halved** by the transformer


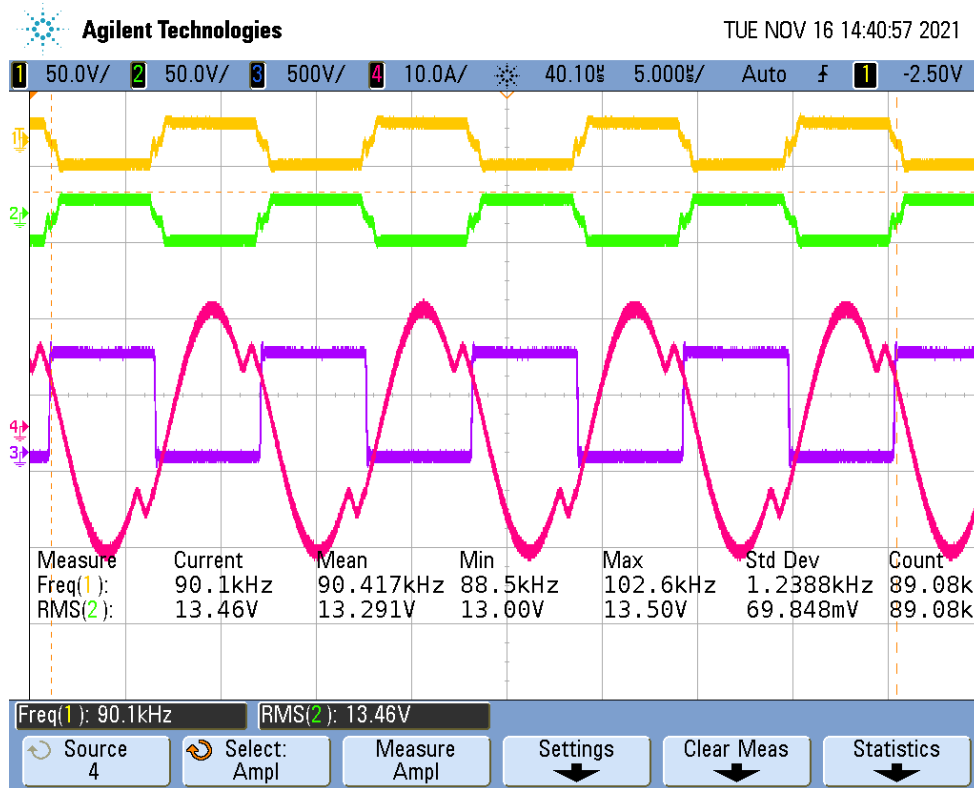
# 6kW DC-DC converter simulation performance (2/4)




800V output, 90kHz

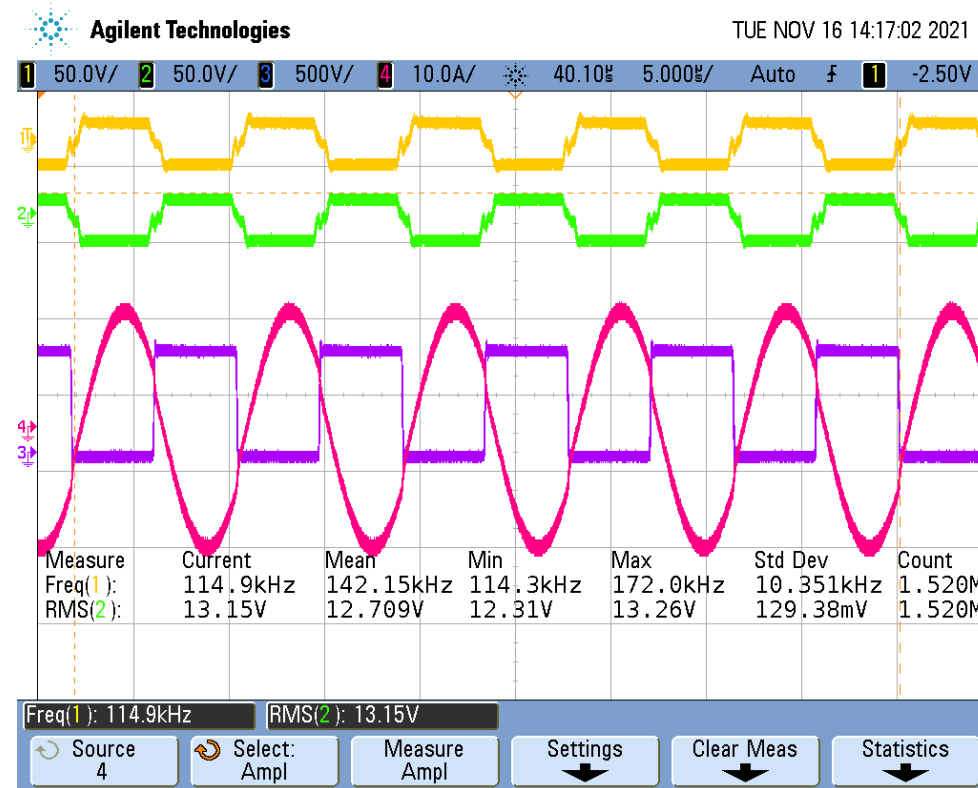


700V output,  
100kHz


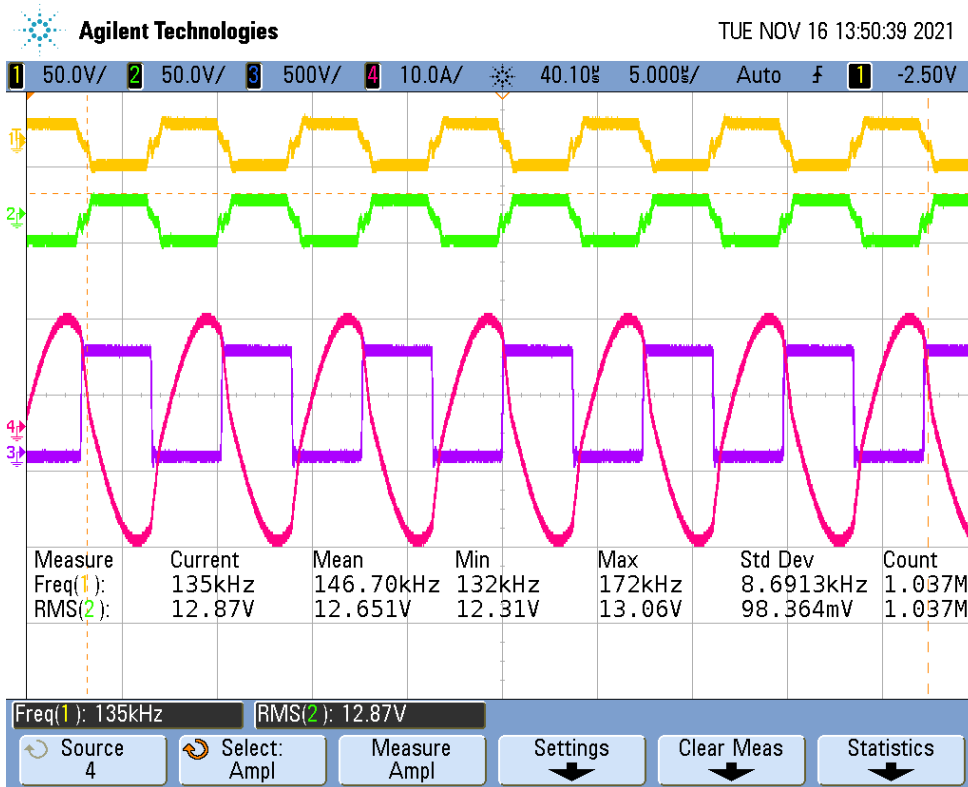
# 6kW DC-DC converter simulation performance (3/4)




500V output,  
135kHz

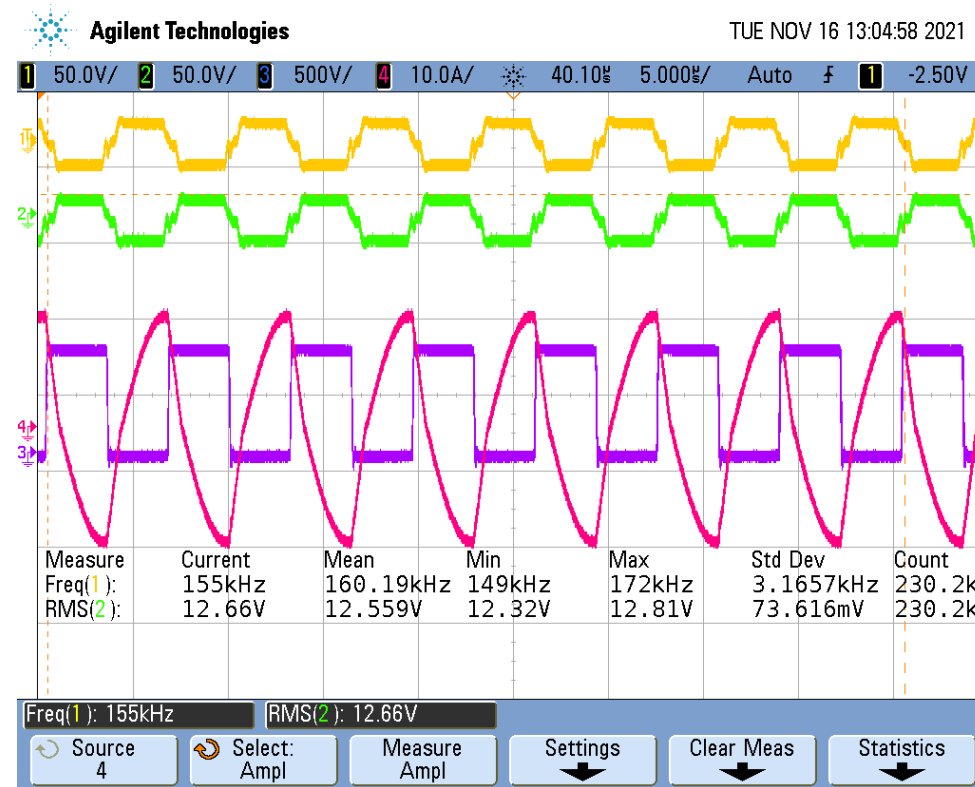


400V output, 145kHz → will  
shift to 90kHz with Bus  
switching scheme
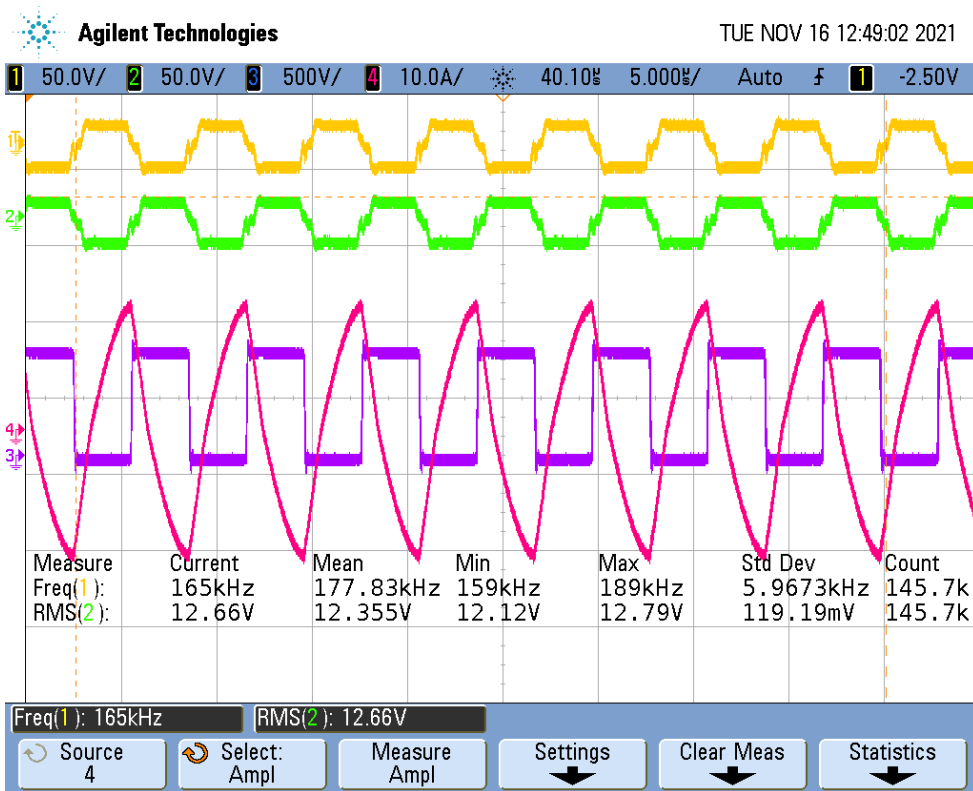
# 6 kW DC-DC converter simulation performance (4/4)



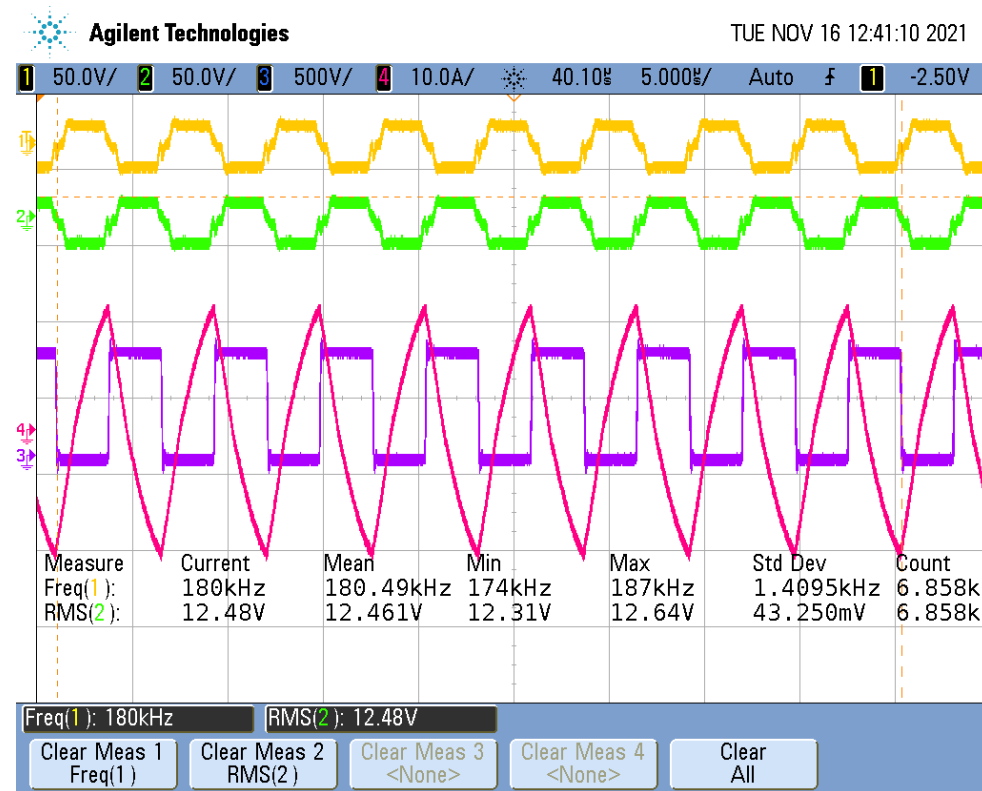300V output, 165kHz  
→ will shift to 120kHz  
with Bus switching  
scheme



200V output, 180kHz  
→ will shift to 130kHz  
with Bus switching  
scheme

# Performance at some typical operating points @Vin ~700V

MOSFET case temperature (worst case) <50C with forced air cooling,  
30 minutes warmup

Vin(V)	Iin(A)	Pin(kW)	Fsw(kHz)	Vout(V)	Iout(A)	Pout(kW)	Efficiency(%)	Load
711.3	3.204	2.2788	180	210.9	9.572	2.0195	88.62120414	21 Ω
706.75	4.943	3.4934	165	307.95	10.413	3.207	91.80168317	28 Ω
704.93	5.515	4.1012	155	396.29	9.791	3.8815	94.64303131	38 Ω
701.57	7.529	5.2827	135	508.47	10.013	5.0929	96.40714029	48 Ω
698.76	9.37	6.5249	115	608.17	10.455	6.3606	97.48195375	54 Ω
702.44	7.049	4.952	100	692.9	6.962	4.825	97.43537964	92 Ω
686.07	8.998	6.1736	90	775.5	4.759	6.019	97.49578852	92 Ω
708.05	4.38	3.1016	115	625.38	4.8583	3.0351	97.85594532	122 Ω

Note efficiency variation under same power condition: mitigated by Vbus select scheme where it operates closer to resonance and higher efficiency. So, for example if we need 300V , operation point will be that of 600V with Vbus(LOW) selected.

# Our technology starts with You



Find out more at [www.st.com](http://www.st.com)

© STMicroelectronics - All rights reserved.

ST logo is a trademark or a registered trademark of STMicroelectronics International NV or its affiliates in the EU and/or other countries.

For additional information about ST trademarks, please refer to [www.st.com/trademarks](http://www.st.com/trademarks).

All other product or service names are the property of their respective owners.



life.augmented